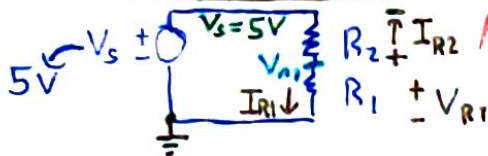



Check out the NVA handout at [eeecs16a.org](http://eeecs16a.org).

NODE VOLTAGE ANALYSIS



Approach: K's equations  
Comp equations (Ohm's, )


- PROCEDURE:
1. choose reference
  2. mark known node voltages
  3. mark unknown node voltages
  4. mark all  $V_{ei}, I_{ei}$
  5. KCL for all nodes w/ unknown V
  6. component equations:  $I_{R1} = \frac{V_{n1}}{R_1}$   $I_{R2} = \frac{V_{R2}}{R_2}$   
replace comp. V with node V:  $V_{R1} = V_{n1} - 0 = V_{n1}$   
 $V_{R2} = V_{n1} - V_s$
  7. substitute:  $I_{R1} = \frac{V_{n1}}{R_1}$   $I_{R2} = \frac{V_{n1} - V_s}{R_2}$
  8. substitute comp. eq into KCL:  $\frac{V_{n1}}{R_1} + \frac{V_{n1} - V_s}{R_2} = 0$
  9. solve for unknown node voltages

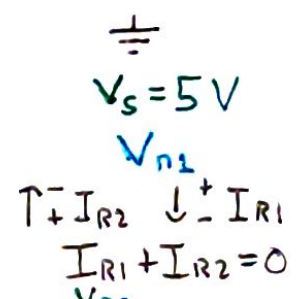

$$V_{n1} = V_s \cdot \frac{R_1}{R_1 + R_2}$$

VOLTAGE DIVIDER

RESISTORS

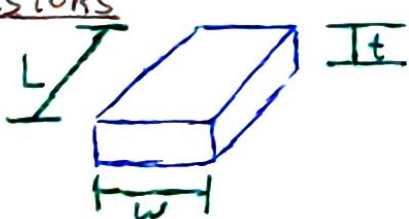


$$R = \rho \cdot \frac{L}{wt}$$

↳ resistivity [ $\Omega \cdot m$ ]

TOUCH SCREEN



what is the voltage at •?

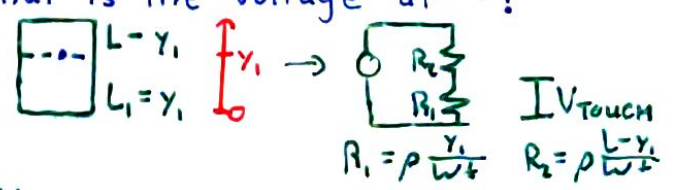


↳ this pixel is  $R = \frac{\rho L}{wt}$


$$V_T = V_s \cdot \frac{R_1}{R_1 + R_2} = \frac{y_1}{L} \cdot V_s$$

# 1D Touch

SIDE VIEW :

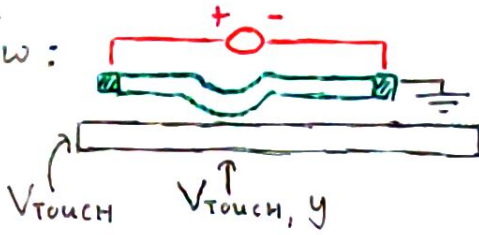


## VOLTMETERS/AMMETERS

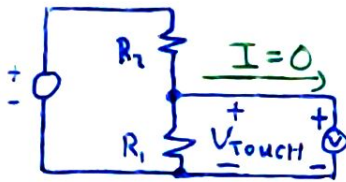

$\rightarrow \# \quad R \rightarrow \infty$

so as to not change the circuit dynamics

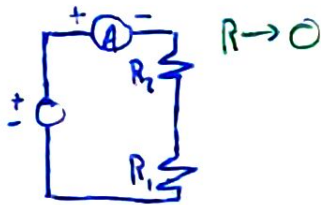

{ Voltmeter  $\rightarrow$  open circuit }  
{ Ammeter  $\rightarrow$  short circuit }