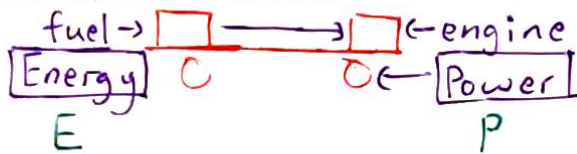


POWER & ENERGY



$P = dE/dt$, which implies
 $E = \int P(t) dt$

ex. 10W light bulb for 1h → $E = 10 \cdot 1 = 10 \text{ Wh} = 36000 \text{ J}$


UNIT $P \rightarrow \text{W}$ $E \rightarrow \text{J} \rightarrow \text{Ws}$
 PG & E charges per kWh.

DEF Batteries store energy, measured in Ah, which isn't a real energy unit

1A → $V_c = 1.5 \text{ V}$ Energy = $V_c \cdot C = 1.5 \text{ V} \cdot 1 \text{ Ah} = 1.5 \text{ Wh}$

1Ah can deliver 1A for 1h, or 0.1A for 10h, etc.

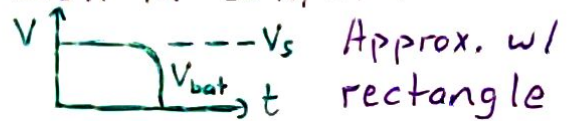Unlike a constant voltage source, a battery will eventually die →



$E, P \rightarrow V, I$


DEF $V_{ab} = dE_{ab}/dq$ the energy required to move q from a to b

DEF charge: electrons (q) Coulombs → $C = 6.2 \cdot 10^{18}$ electrons

DEF $I = dq/dt$ $1 \text{ A} = 1 \text{ C/s}$


DEF $P = dE/dt = dE/dq \cdot dq/dt = VI$ most important of these 4 eqs

PASSIVE SIGN CONVENTION

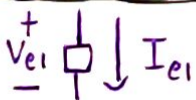

$P_{diss} = V_{ei} \cdot I_{ei}$
 ↳ Power dissipated

$P_{diss} < 0$ is power delivery

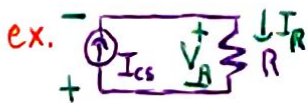

$I_{cs} = 1 \text{ mA}$

$V_R = RI_R = 1 \cdot 1 = 1 \text{ A}\Omega = 1 \text{ V}$


$R = 1 \text{ k}\Omega$

$P_R = V_R I_R = 1 \text{ V} \cdot 1 \text{ mA} = 1 \text{ mW diss.}$

$V_{cs} + V_R = 0 \rightarrow V_{cs} = -V_R$

$P_{cs} = -1 \text{ V} \cdot 1 \text{ mA} = -1 \text{ mW deliv.}$

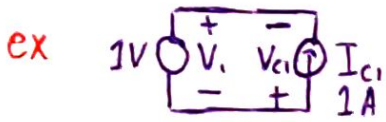$P_R + P_{cs} = 0$ conservation of energy



$$-V_i - V_{cl} = 0$$

$$V_{cl} = -V_i$$


$$P_{cl} = -1V \cdot 1A = -1W$$

$$P_{vs} = V_i \cdot I_{cl} = 1W \quad \Sigma = 0$$

if this isn't a rechargeable V_s , 4th of July may come early

2D TOUCH SCREEN

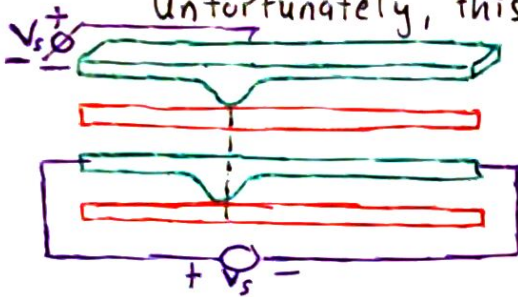Two stacked 1D screens with an insulator in between!
 Unfortunately, this isn't a very functional method.



merge the red layers & alternate $V_s \rightarrow$ down to 3 layers.
 why stop at 3 layers?

