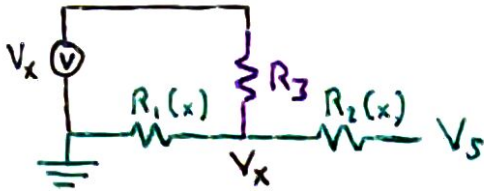



RECAP: 2D Touch



this is essentially an open circuit, so R_3 won't be a problem

to measure V_y , simply switch colors!




EQUIVALENCE

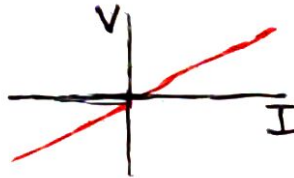

The equivalent resistance of resistors in series is the sum of these resistances. Prove with KVL.

The equivalent resistance R_{eq} of n resistors in parallel is $\frac{1}{R_{eq}} = \sum_{i=1}^n \frac{1}{R_i}$. Prove with KCL.


AMPLIFIERS

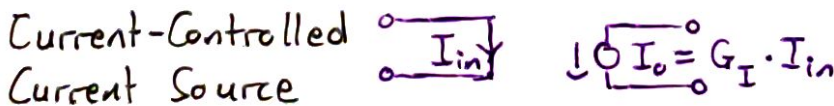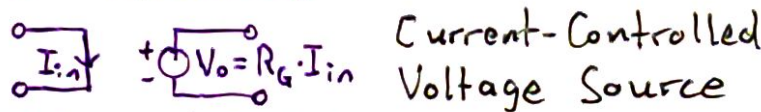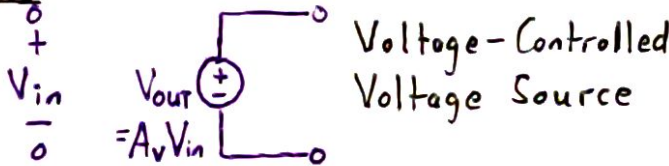


SUPERPOSITION

NVA: $[Y] \cdot \nabla_n = \text{constant sources} \cdot [Y]^{-1} = \nabla_n$

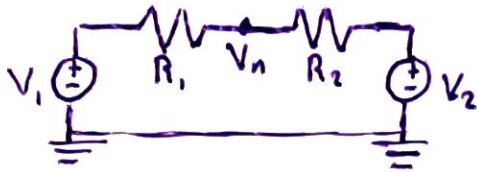An easier method is linear superposition. See next page & EECS 16B.



1. zero all but 1 source
2. repeat for diff. source
3. keep repeating for all sources
4. sum results

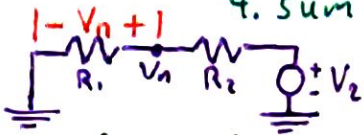1. zero V_1 :  $V_n = \frac{V_2 \cdot R_1}{R_1 + R_2}$

2. zero V_2 : $V_n = (V_1 \cdot R_2) \div (R_1 + R_2)$

3. sum both: $\frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$