
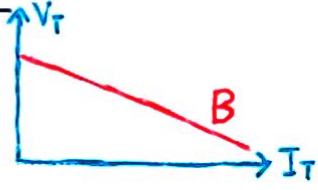


Ideal V_s cannot produce A, as it isn't a battery and constantly produces the same V . The relationship between V & I must be linear, as given by $A \vec{v}_n = \vec{b} \rightarrow \vec{v}_n = A^{-1} \vec{b}$, as shown in B or C. The latter, however, only occurs with no V_s present.


Of the given IV curves, only curve B may depict the circuit.

THEVENIN EQUIVALENT CIRCUIT

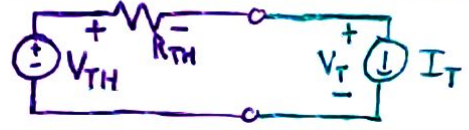

$V_{oc} = V_{TH}$
 $I_{sc} = V_{TH}/R_{TH}$

NORTON EQUIVALENT CIRCUIT

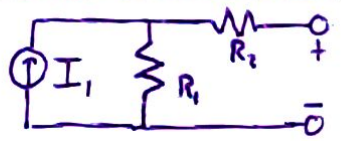


$V_{oc} = R_1 I_1$
 $I_{sc} = I_1 \frac{R_1}{R_1 + R_2}$



$V_{TH} = R_1 I_1$
 $R_{TH} = \frac{V_{TH}}{I_{sc}} = R_1 + R_2$

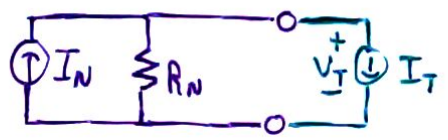Realize that the above circuits have the same IV curves



$V_{oc} = I_N R_N$
 $I_{sc} = I_N$ } convert to Thevenin { $V_{TH} = I_N R_N$
 $R_{TH} = V_{TH}/I_N = R_N$
 these 2 circuits (T,N) are equivalent!

CIRCUIT ANALYSIS SUMMARY

- KVL, KCL
 - Ohm's Law
 - Node Voltage Analysis
 - Equivalence
 - Superposition
- | Basics
- | Universal Procedure