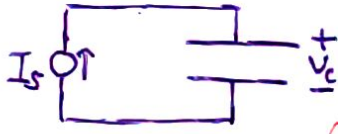


VIRTUAL EXPERIMENT



$Q_c = C \cdot V_c \rightarrow$ Voltage charged \rightarrow Capacitance

UNIT Capacitance [F] \rightarrow Farad

$C = \epsilon \cdot \frac{A}{d}$

$\epsilon =$ permittivity

$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

$\epsilon = \epsilon_0 \cdot \epsilon_r$

$\epsilon_r (\text{air}) = 1$

$\epsilon_r (\text{water}) = 80$

CAPACITOR I/V

$Q = CV$


$I = dq/dt = C \cdot dV/dt$

$I = C \cdot dV/dt$



$V_s = V_c = \text{constant}$
 $I = C \cdot 0 = 0$


steady state
 $dV/dt = dI/dt = 0$

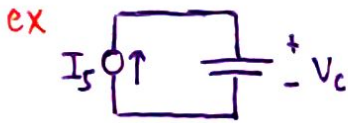

$I_c = I_s = C \cdot dV/dt$
 $dV_c/dt = I_s/C$


$V_c = (I_c/C) \cdot t + V_{c0} \rightarrow V_c(t=0) = V_{c0}$

MEMORY

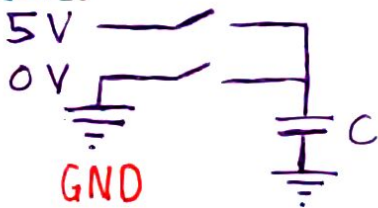

This is how DRAM works (per byte)

EQUIVALENCE

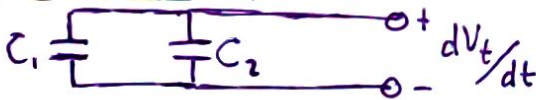

$I_{C1} = C_1 \cdot \frac{dV_{C1}}{dt} = C_1 \cdot \frac{dV_t}{dt}$
 $I_{C2} = C_2 \cdot \frac{dV_{C2}}{dt}$ $C_{eq} = \frac{I_{C1} + I_{C2}}{dV_t/dt}$

for 2 capacitors in parallel, $C_{eq} = C_1 + C_2$

for 2 capacitors in series, $C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = C_1 || C_2$