

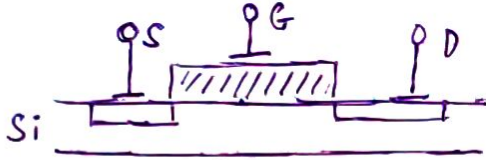


TRANSISTORS

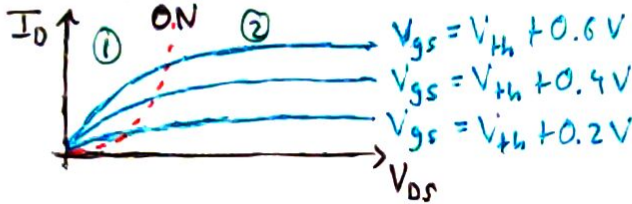MOSFET: Metal Oxide Semiconductor Field Effect Transistor



S: source
G: gate
D: drain

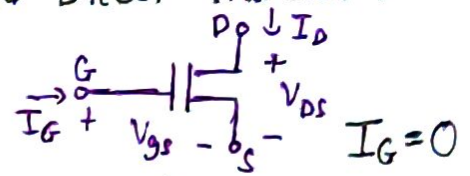


$V_{GS} = 0$
 $V_{GS} < V_{TH}$ } OFF ①
Let $V_{TH} = [0.2, 0.3]V$

- 0. OFF $V_{GS} < V_{TH}$
 - 1. ON $V_{GS} > V_{TH}$ region near origin; "linear region"
 - 2. ON $V_{GS} > V_{TH}$ region to the right; "saturation"
- Regions 0 & 1 are good for implementing a switch.
Region 2 is good for implementing current sources, amplifiers, .., analog functions.


NMOS (1st MOSFET)

PMOS (2nd MOSFET)

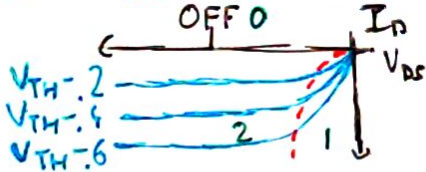
see diagram & cross-section above
cross-sec same, materials inverted
 $V_{DS} \leq 0$ $I_D \leq 0$ $V_{TH} : [-0.3, -0.2]V$
at OFF, $V_{GS} = 0$, $V_{GS} \geq V_{TH}$




CMOS (complementary): has NMOS & PMOS

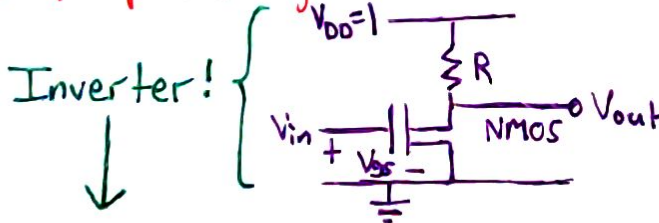

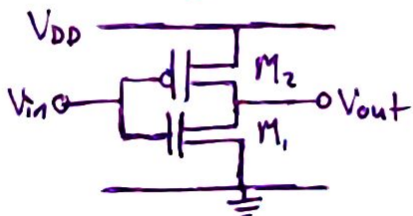$V_{in} = 0 \implies V_{out} = V_{DD}$ OFF
 $V_{in} = V_{DD} \implies V_{out} = 0$ ON
@ ON, $I_D = V_{DD}/R$, $P = I_D V_{DD}$



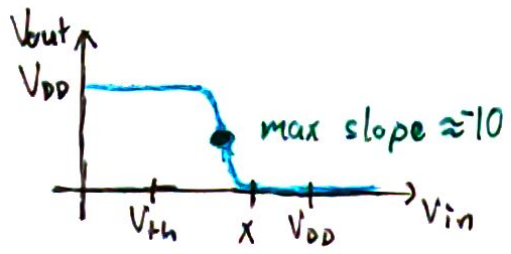$V_{in} = V_{DD} \implies V_{GS1} = V_{DD} > V_{TH} \implies M_1$ ON
 $\implies V_{GS2} = 0 \implies M_2$ OFF
 $V_{in} = 0 \implies V_{GS1} = 0, V_{GS2} = -V_{DD} \implies$ reverse



$$x = V_{DD} - |V_{th2}|$$