

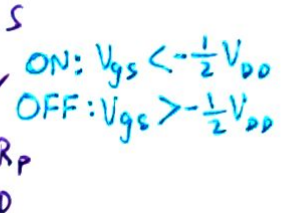


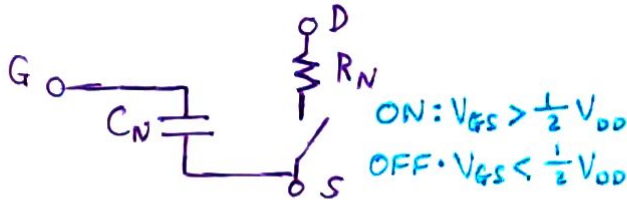


We'll model transitions between ON & OFF as occurring at $V_{GS} = \frac{1}{2} V_{DD}$.


Thus, we can simplify NMOS:

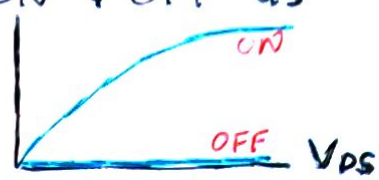

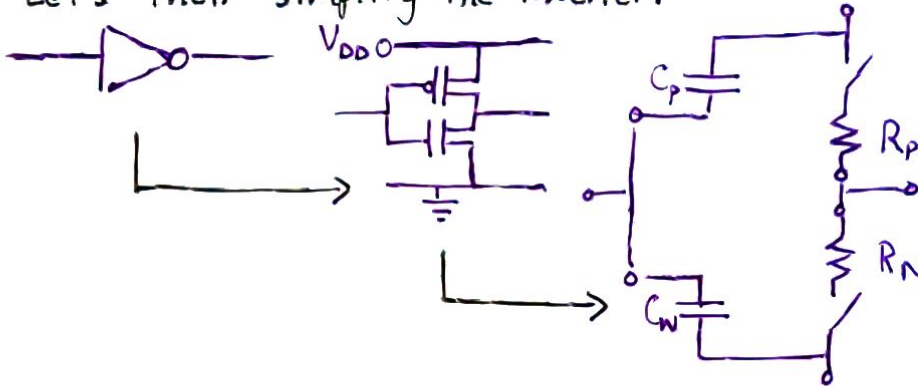Analogously for the PMOS:
Let's then simplify the inverter:



What if we chain inverters?

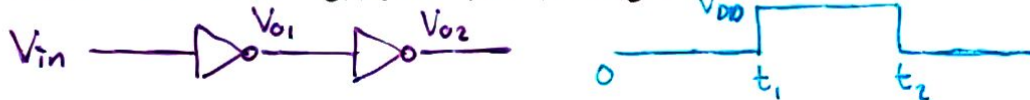

Before t_1 , V_{o1} is high, V_{in} & V_{o2} are low

After t_1 , $\frac{V_{o1}}{R_N} + C_N \frac{d}{dt} V_{o1} + C_P \frac{d}{dt} (V_{o1} - V_{DD}) = 0$
 $\frac{d}{dt} V_{o1} + \frac{1}{R_N} (C_N + C_P) V_{o1} = 0 \quad V_{o1}(t_1) = V_{DD}$

↳ time constant: $\Omega \cdot F = \text{seconds } \tau$

$\frac{d}{dt} V_{o1} = -\frac{1}{\tau} V_{o1} \quad -\frac{1}{\tau} = \lambda \quad \text{eigenvalues??}$

$\frac{d}{dt} V_{o1} = \lambda V_{o1} \quad V_{o1}(t_1) = V_{DD}$

$V_{o1} = A e^{\lambda t} \rightarrow A e^{\lambda t} \Big|_{t_1} = A e^{\lambda t_1} = V_{DD} \quad A = V_{DD} e^{-\lambda t_1}$

$V_{o1} = V_{DD} e^{-\lambda t_1} \cdot e^{\lambda t}$

Just solved a differential equation!