

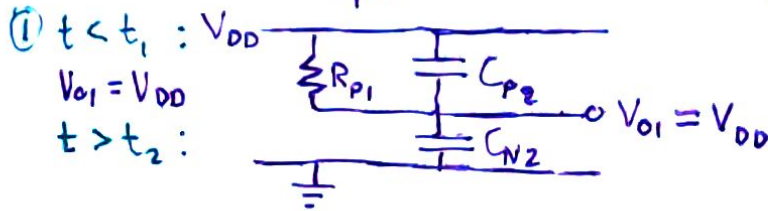


EECS 16B ## 1.30 LECTURE 4

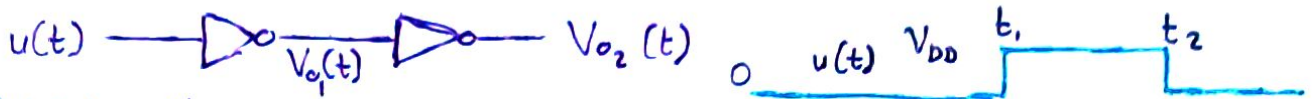


$$\tau_P = R_{P1} (C_{P2} + C_{N2})$$

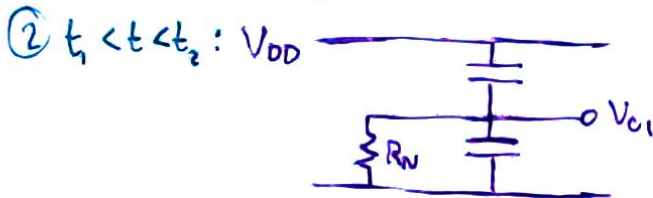

$$\tau_N = R_N (C_P + C_N)$$

At ①, $\frac{d}{dt} V_{o1} = -(R_P (C_N + C_P))^{-1} \cdot V_{o1} + V_{DD} (R_P (C_N + C_P))^{-1}$

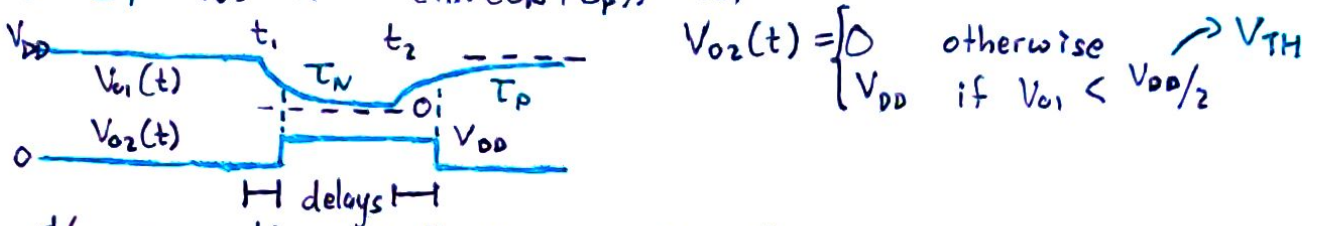At ②, $\frac{d}{dt} V_{o1} = -(R_N (C_N + C_P))^{-1} \cdot V_{o1}$



$$\frac{d}{dt} v = -\frac{1}{\tau} v + \frac{1}{\tau} \frac{V_{DD}}{\text{external}} \quad \lambda = -\frac{1}{\tau}$$

RULE: 1st order — only variable, only 1st derivative
 — RHS has a constant external input

$v(t_0)$ is defined

$$v = v_{\infty} + (v(t_0) - v_{\infty}) e^{-\frac{t-t_0}{\tau}}$$

$$v(t_0) = v_{\infty} + (v(t_0) - v_{\infty}) \cdot 1$$

AUDIO AMP: RC CIRCUIT



$$\frac{d}{dt} V_o = -\frac{1}{RC} V_o + \frac{1}{RC} V_{in}(t)$$

$$V_{in} = V_{in} \cdot e^{st}$$

eigenfunction for I/O behavior

in a real amp, R would be a potentiometer/knob

$$V_o(t) = V_o \cdot e^{st}$$

$$s V_o e^{st} = -\frac{1}{RC} V_o e^{st} + \frac{1}{RC} V_{in} e^{st}$$

$$s V_o + \frac{1}{RC} V_o = \frac{1}{RC} V_{in}$$

$$V_o = \frac{1}{RC} (s + \frac{1}{RC})^{-1} \cdot V_{in} = (1 - s/\lambda)^{-1} \cdot V_{in}$$

$$v_o(t) = (1 - s/\lambda)^{-1} \cdot V_{in} \cdot e^{st}$$