

ANALYSIS



$v_{in}(t) = \underbrace{V_{in}}_{\text{real}} \cos \omega t = \text{Re}[V_{in} e^{j\omega t}]$

$v_o(t) = \text{Re}[\underbrace{V_o}_{\text{complex}} e^{j\omega t}]$

Voltage Divider!
 $V_o/V_{in} = H(j\omega) = (j\omega C)(j\omega C + R + j\omega L)^{-1}$
 transfer


RECALL: TIME DOMAIN ANALYSIS

$A = \begin{bmatrix} 0 & 1/L \\ -1/C & -R/L \end{bmatrix}$

$\det(\lambda I - A) = \lambda^2 + R/L \lambda + 1/LC$

$\lambda_{1,2} = -\frac{1}{2} \frac{R}{L} \pm \sqrt{(\frac{1}{2} \frac{R}{L})^2 - \frac{1}{LC}}$ may be complex

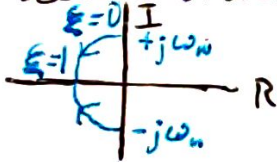For second-order systems, $\omega_n = \sqrt{1/LC}$ & $\xi = \frac{1}{2} R/\sqrt{LC}$
 ↳ greek letter Xi



$\lambda_{1,2} = -\xi \omega_n \pm j\omega_n \sqrt{1-\xi^2}$
 time waveform: $e^{\lambda t} = e^{-\xi \omega_n t} \text{Re}[e^{j\omega_n t \sqrt{1-\xi^2}}]$



$T = 2\pi \cdot (\omega_n \sqrt{1-\xi^2})^{-1}$

FREQUENCY DOMAIN

Single frequency ω , phasor analysis w/ simplified ω_n & ξ


$\frac{V_o}{V_{in}} = H(j\omega) = \frac{\omega_n^2}{(j\omega)^2 + (j\omega)2\xi\omega_n + \omega_n^2}$

Bode Plot:


1. Low freq.: $\omega \ll \omega_n$ $H(j\omega) \approx 1$

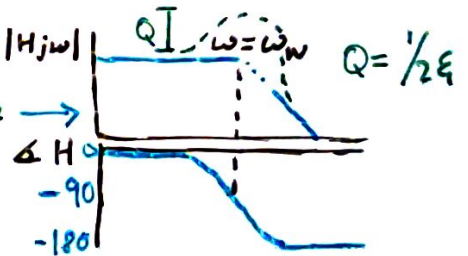2. High freq.: $\omega \gg \omega_n$ $H(j\omega) \approx -\omega_n^2/\omega^2$

$H(j\omega_n) = \omega_n^2 / (j2\xi\omega_n^2) = -j/2\xi$



POSSIBLE APPLICATIONS

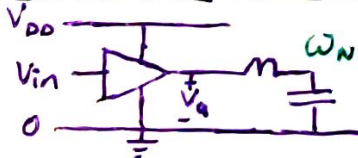

$-|V_o| = \frac{1}{2\xi} |V_{in}|$